
Lab 8

Shiyu Wang

Hao Jiang


8.1

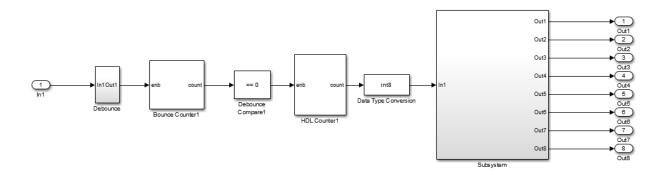


Where In1Out1 is the push button on/off from lab6.

And the subsystem is the bit slicer.

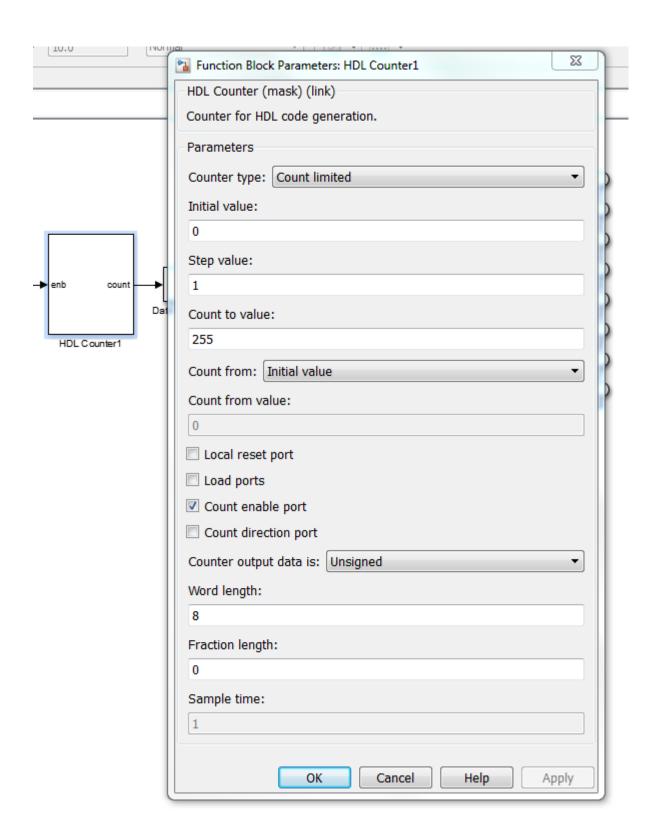We want the counter to count as 2Hz, which means 2 cycles per second. Since the HDL counter will be counting at a frequency of 50 MHz. We will set the bounce Counter count from 0 to 25000000.




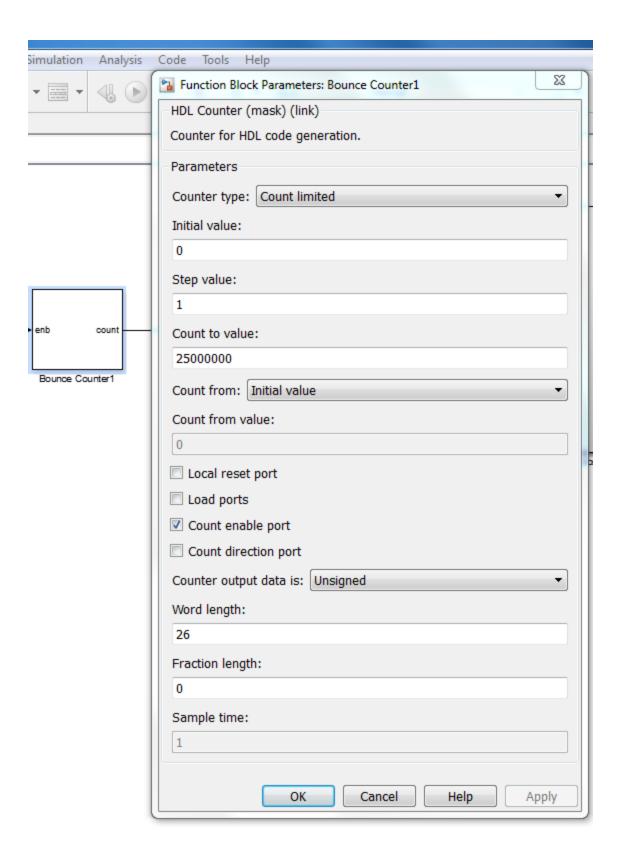

## Set Target Interface: Use the center button to control the LEDs to stop/run


Port Name	Port Type	Data Type	Target Platform Interfaces	Bit Range / Address / FPGA Pin
In1	Inport	boolean	Push Buttons L-R-U-D-S [0:4] ▼	[4]
Out1	Outport	ufix1	LEDs General Purpose [0:7] ▼	[0]
Out2	Outport	ufix1	LEDs General Purpose [0:7] ▼	[1]
Out3	Outport	ufix1	LEDs General Purpose [0:7] ▼	[2]
Out4	Outport	ufix1	LEDs General Purpose [0:7] ▼	[3]
Out5	Outport	ufix1	LEDs General Purpose [0:7] ▼	[4]
Out6	Outport	ufix1	LEDs General Purpose [0:7] ▼	[5]
Out7	Outport	ufix1	LEDs General Purpose [0:7] ▼	[6]
Out8	Outport	ufix1	LEDs General Purpose [0:7] ▼	[7]

## 8.2

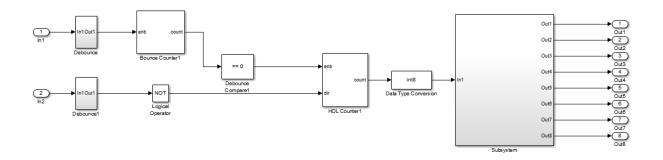

Set Target Interface: Use the center button to control the LEDs to stop/run; Use the right button to change the direction.

Port Name	Port Type	Data Type	Target Platform Interfaces	Bit Range / Address / FPGA Pin
In1	Inport	boolean	Push Buttons L-R-U-D-S [0:4] ▼	[4]
In2	Inport	boolean	Push Buttons L-R-U-D-S [0:4] ▼	[1]
Out1	Outport	ufix1	LEDs General Purpose [0:7] ▼	[0]
Out2	Outport	ufix1	LEDs General Purpose [0:7] ▼	[1]
Out3	Outport	ufix1	LEDs General Purpose [0:7] ▼	[2]
Out4	Outport	ufix1	LEDs General Purpose [0:7] ▼	[3]
Out5	Outport	ufix1	LEDs General Purpose [0:7] ▼	[4]
Out6	Outport	ufix1	LEDs General Purpose [0:7] ▼	[5]
Out7	Outport	ufix1	LEDs General Purpose [0:7] ▼	[6]
Out8	Outport	ufix1	LEDs General Purpose [0:7] ▼	[7]

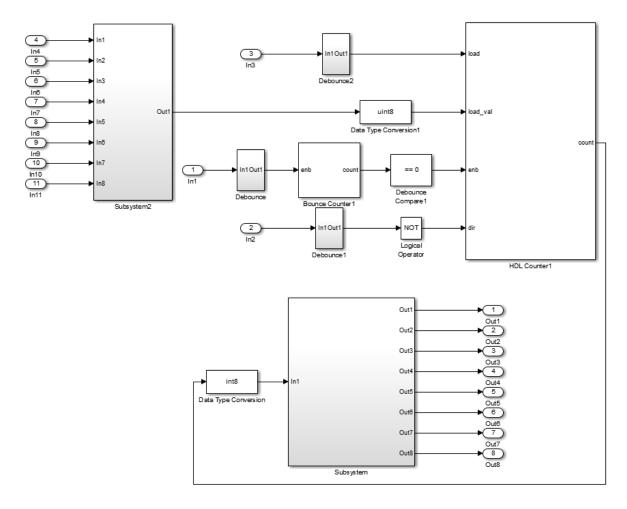

Subsystem2 is from the previous lab which load the switch and then we translate it into the load value.

Set Target Interface: Use the center button to control the LEDs to stop/run; Use the right button to change the direction. Use the left button to load the switch.


In1	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	▼.	[4]
In2	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	▼)	[1]
In3	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	▼)	[0]

In4	Inport	boolean	DIP Switches [0:7]	▼ [7]
In5	Inport	boolean	DIP Switches [0:7]	▼ [6]
In6	Inport	boolean	DIP Switches [0:7]	▼ [5]
In7	Inport	boolean	DIP Switches [0:7]	▼ [4]
In8	Inport	boolean	DIP Switches [0:7]	▼ [3]
In9	Inport	boolean	DIP Switches [0:7]	▼ [2]
In10	Inport	boolean	DIP Switches [0:7]	▼ [1]
In11	Inport	boolean	DIP Switches [0:7]	▼ [0]

Where input 4 is corresponding to the highest digit and input 11 is the lowest digit.

Out1	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [0]
Out2	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [1]
Out3	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [2]
Out4	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [3]
Out5	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [4]
Out6	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [5]
Out7	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [6]
Out8	Outport	ufix1	LEDs General Purpose [0:7]	▼ [7]

## 8.4

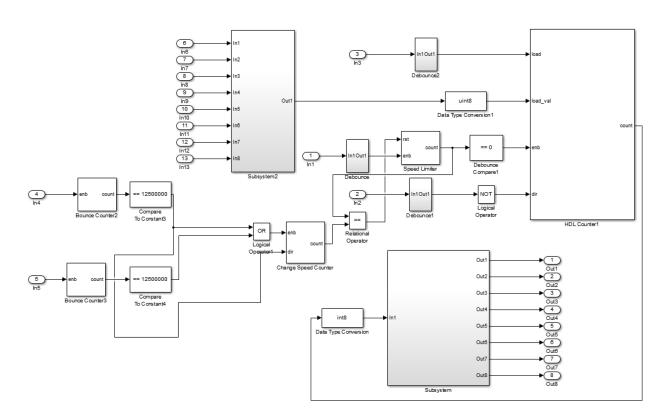

In1	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	<b>-</b> [4]
In2	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	<b>[1]</b>
In3	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	<b>▼</b> [0]
In4	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	▼ [3]
In5	Inport	boolean	Push Buttons L-R-U-D-S [0:4]	▼ [2]
In6	Inport	boolean	[DIP Switches [0:7]	<b>▼</b> ][7]
In7	Inport	boolean	DIP Switches [0:7]	<b>▼</b> [6]
In8	Inport	boolean	DIP Switches [0:7]	▼ [5]
In9	Inport	boolean	DIP Switches [0:7]	▼ [4]
In 10	Inport	boolean	DIP Switches [0:7]	<b>[3]</b>
In11	Inport	boolean	DIP Switches [0:7]	▼ [2]
In12	Inport	boolean	DIP Switches [0:7]	<b>[1]</b>
In13	Inport	boolean	DIP Switches [0:7]	<b>[</b> 0]
			[	
Out1	Outport	ufix1	LEDs General Purpose [0:7]	[0]
Out2	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [1]
Out3	Outport	ufix1	[LEDs General Purpose [0:7]	<b>v</b> [2]
Out4	Outport	ufix1	LEDs General Purpose [0:7]	▼ [3]
Out5	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [4]
Out6	Outport	ufix1	LEDs General Purpose [0:7]	▼ [5]
Out7	Outport	ufix1	LEDs General Purpose [0:7]	<b>▼</b> [6]
Out8	Outport	ufix1	LEDs General Purpose [0:7]	[7]

.